

ECE 351

Verilog and FPGA Design

Week 7_1: Blocking and non-blocking assigns (revisited)
Modeling sequential logic

Roy Kravitz
Electrical and Computer Engineering Department
Maseeh College of Engineering and Computer Science

What did you think of the midterm?

Problem 1 solution: ..\..\exams\midterm_exam\solution_code\sync_ctr_mt

Blocking and non-blocking assignments (Revisited)

Blocking vs. non-blocking assignment

- The SystemVerilog standard allows always blocks to be scheduled in any order
 - If the 1st block executes first, the 2nd block will calculate Out based on the new value of Sel
 - If the 2nd block executes first, it will use the old value of Sel to calculate Out
- Solutions include using non-blocking assignment or putting both functions in the same block

```
always_ff @(posedge clk)
begin
    Sel = In0;
end
```


```
always_ff @(posedge clk)
begin
    if (Sel == 1)
        Out = PB;
    else
        Out = 1'b0;
end
```

Blocking vs. non-blocking assignment (cont'd)⁶

 - Examples from Cliff Cummings' excellent paper on non-blocking assignments (used with permission of the author)

Download the paper from the [Course Content/Other Readings Interesting Articles/CummingsSNUG2000SJ_NBA](#)

- Suppose you want to write SystemVerilog for the three-stage pipeline register below




Blocking assignment: Example #1

```

module pipeb1 (q3, d, clk);
  output logic [7:0] q3;
  input logic [7:0] d;
  input logic clk;
  logic [7:0] q3, q2, q1;
  always_ff @(posedge clk) begin
    q1 = d;
    q2 = q1;
    q3 = q2;
  end
endmodule

```

 


intermediate stages are optimized out because they are within a single always block and even though the statements are blocking, the minimized equation is $q3 = d$;

On every clock rising edge the value of d is transferred directly to q3 without delay!

Blocking assignment: Example #2
 
```
module pipeb2 (q3, d, clk);  
  output logic [7:0] q3;  
  input logic [7:0] d;  
  input logic clk;  
  logic [7:0] q3, q2, q1;  
  always_ff @(posedge clk) begin  
    q3 = q2;  
    q2 = q1;  
    q1 = d;  
  end  
endmodule
```




Changing the order of blocking assignments within a clocked always block yields dramatically different results!

Blocking assignment: Example #3

```

module pipeb3 (q3, d, clk);
  output logic [7:0] q3;
  input logic [7:0] d;
  input logic clk;
  logic [7:0] q3, q2, q1;
  always_ff@ (posedge clk) q1=d ;
  always_ff@ (posedge clk) q2=q1;
  always_ff@ (posedge clk) q3=q2;
endmodule


```

 

...but simulation results are unpredictable because the three always blocks can be executed in any order

Blocking assignment: Example #4
 
```
module pipeb4 (q3, d, clk);  
  output [7:0] q3;  
  input  [7:0] d;  
  input  clk;  
  reg [7:0] q3, q2, q1;  
  always@ (posedge clk) q3=q2;  
  always@ (posedge clk) q2=q1;  
  always@ (posedge clk) q1=d;  
endmodule
```



Simulation results are unpredictable just as before

Non-blocking assignment: Examples #1, #2 ¹¹

When each of the four blocking-assignment examples are rewritten with non-blocking assignments, all four simulate correctly and synthesize correctly

```
module pipen1 (q3, d, clk);
  output logic [7:0] q3;
  input  logic [7:0] d;
  input logic  clk;
  logic [7:0] q3, q2, q1;
  always_ff @(posedge clk) begin
    q1 <= d;
    q2 <= q1;
    q3 <= q2;
  end
endmodule
```

```
module pipen2 (q3, d, clk);
  output logic [7:0] q3;
  input logic  [7:0] d;
  input logic  clk;
  logic [7:0] q3, q2, q1;
  always_ff @(posedge clk) begin
    q3 <= q2;
    q2 <= q1;
    q1 <= d;
  end
endmodule
```

ECE 351 Verilog and FPGA Design

Non-blocking assignment: Examples #3, #4 ¹²

```
module pipen3 (q3, d, clk);
  output logic [7:0] q3;
  input logic [7:0] d;
  input logic clk;
  logic [7:0] q3, q2, q1;
  always_ff @(posedge clk) q1<=d ;
  always_ff @(posedge clk) q2<=q1;
  always_ff @ posedge clk) q3<=q2;
endmodule
```

```
module pipen4 (q3, d, clk);
  output logic [7:0] q3;
  input logic [7:0] d;
  input logic clk;
  logic [7:0] q3, q2, q1;
  always_ff @(posedge clk) q3<=q2;
  always_ff @(posedge clk) q2<=q1;
  always_ff @(posedge clk) q1<=d;
endmodule
```

ECE 351 Verilog and FPGA Design

Blocking vs. non-blocking scoreboard

- Which of the 4 blocking and 4 nonblocking examples are guaranteed to simulate and synthesize correctly?

Example	Blocking		Nonblocking	
	Sim	Synth	Sim	Synth
1	No	No	Yes	Yes
2	Yes	Yes	Yes	Yes
3	No	Yes	Yes	Yes
4	No	Yes	Yes	Yes

Which assignment should I use?

☐ Recommended:

- Use non-blocking assignments for modeling clocked processes in sequential logic.
- Use blocking assignments for modeling combinational logic

Modeling sequential logic

Source material drawn from:


- Roy's ECE 351 and ECE 571 lecture material
- *RTL Modeling with SystemVerilog* by Stuart Sutherland
- *Logic Design and Verification Using SystemVerilog* by Donald Thomas

Shift registers and counters

Sources:

- Roy's lecture notes from days long past (2003 – 2004)
- *Fundamentals of Digital Logic with Verilog 1st Edition*, Stephen Brown and Zvonko Vranesic, McGraw-Hill, 2003

Shift registers

 

A Shift register using 4 D flip-flops

```

module shiftreg4 (
    input logic In, Clock
    output Out
);
    logic [1:4] Q;

    assign Out = Q[4];
    always_ff @(posedge Clock)
        Q <= {In, Q[1:3]};


endmodule

```

	In	Q ₁	Q ₂	Q ₃	Q ₄ = Out
t_0	1	0	0	0	0
t_1	0	1	0	0	0
t_2	1	0	1	0	0
t_3	1	1	0	1	0
t_4	1	1	1	0	1
t_5	0	1	1	1	0
t_6	0	0	1	1	1
t_7	0	0	0	1	1

Parallel access shift register

Loads input or shifts on clock edge

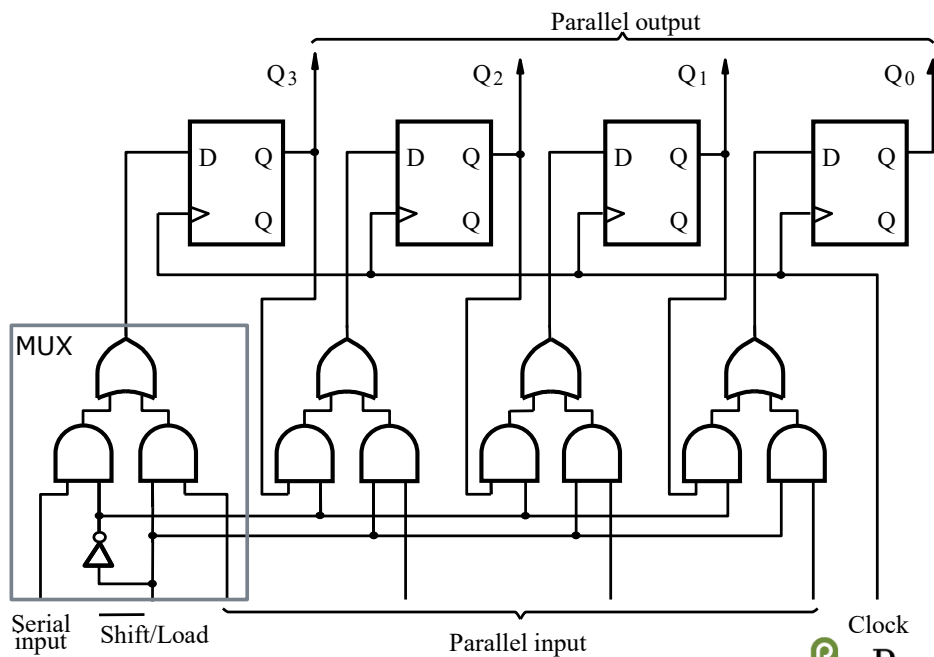

Parallel access shift register (cont'd)

D flip-flop with a 2-to-1 multiplexer on the D input

```
module muxdff (
    input logic D0, D1, Sel, Clock,
    output logic Q
);
    always_ff @(posedge Clock)
        if (!Sel)
            Q <= D0;
        else
            Q <= D1;
endmodule: muxdff
```

Four-bit shift register

```
module shift4 (
    input logic [3:0] R,
    input logic L, w, Clock,
    output logic [3:0]
);

    muxdff Stage3 (w, R[3], L, Clock, Q[3]);
    muxdff Stage2 (Q[3], R[2], L, Clock, Q[2]);
    muxdff Stage1 (Q[2], R[1], L, Clock, Q[1]);
    muxdff Stage0 (Q[1], R[0], L, Clock, Q[0]);
```

```
endmodule: shift4
```

ECE 351 Verilog and FPGA Design

Parallel access shift register (cont'd)

Alternate code for a four-bit shift register

```
module shift4 (  
    input logic [3:0] R,  
    input logic L, w, Clock,  
    output logic [3:0] Q  
);  
  
    always_ff @(posedge Clock)  
        if (L)  
            Q <= R;  
        else begin  
            Q[0] <= Q[1]; // Could also be Q <= {w, Q[3:1]};  
            Q[1] <= Q[2];  
            Q[2] <= Q[3];  
            Q[3] <= w;  
        end  
  
endmodule: shift4
```

An n -bit parameterized shift register

```
module shiftn
#( parameter n = 16)
(
    input logic [n-1:0] R,
    input logic L, w, Clock,
    output logic [n-1:0] Q
);


    logic [n-1:0] Q;

    always_ff @(posedge Clock)
        if (L)
            Q <= R;
        else begin
            for (int k = 0; k < n-1; k = k+1) begin
                Q[k] <= Q[k+1];
                Q[n-1] <= w;
            end
        end
end
```

endmodule: shiftn

ECE 351 Verilog and FPGA Design

Asynchronous Up-Counter

 

Synchronous Up-counter

A large asynchronous counter can be very slow as the toggle propagates through all the bits

A synchronous counter provides a much Cleaner design

Bit n toggles if all lower significant bits are 1

Clock cycle	Q2	Q1	Q0
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0

Q1 changes

Q2 changes

Synchronous Up-counter (cont'd)

```
module upcount (  
    input logic Resetn, Clock, E  
    output logic [3:0] Q  
);  
    logic [3:0] Q;  
  
    always_ff @(negedge Resetn or posedge Clock)  
        if (!Resetn)  
            Q <= 4'b0;  
        else if (E)  
            Q <= Q + 1'b1;  
        else  
            Q <= Q;  
  
endmodule: upcount
```

Synchronous counter with parallel load

```
module upcount (  
    input logic [3:0] R,  
    input logic Resetn, Clock, E, L,  
    output logic [3:0] Q  
);  
    logic [3:0] Q;  
  
    always_ff @(negedge Resetn or posedge Clock)  
        if (!Resetn)  
            Q <= 0;  
        else if (L)  
            Q <= R;  
        else if (E)  
            Q <= Q + 1;    // for a down counter Q <= Q - 1;  
        else  
            Q <= Q;  
  
endmodule
```


Up/Down counter w/ parallel load


```
module updowncount
#(parameter n = 8)
(
    input logic [n-1:0] R,
    input logic Clock, L, E, up_down,
    output logic [n-1:0] Q
);
    logic [n-1:0] Q;
    logic direction;

    always_ff @(posedge Clock) begin
        direction = up_down ? 1 : -1;


        if (L)
            Q <= R;
        else if (E)
            Q <= Q + direction;
    end

endmodule: updowncount
```

Other counters – Ring counter

 

(a) An n -bit ring counter

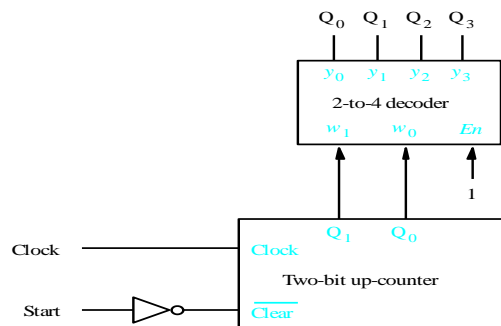

(b) A four-bit ring counter


A ring-counter moves a 1 around a "ring" of latches:

1000->
0100->
0010->
0001->
1000 ...

A "one-hot" encoding

Other counters – Johnson counter


30

 

Johnson counter: 0000 -> 1000 -> 1100 -> 1110 ->
1111 -> 0111 -> 0011 -> 0001 -> 0000 ->

Gray Code counter/mux revisited on last time

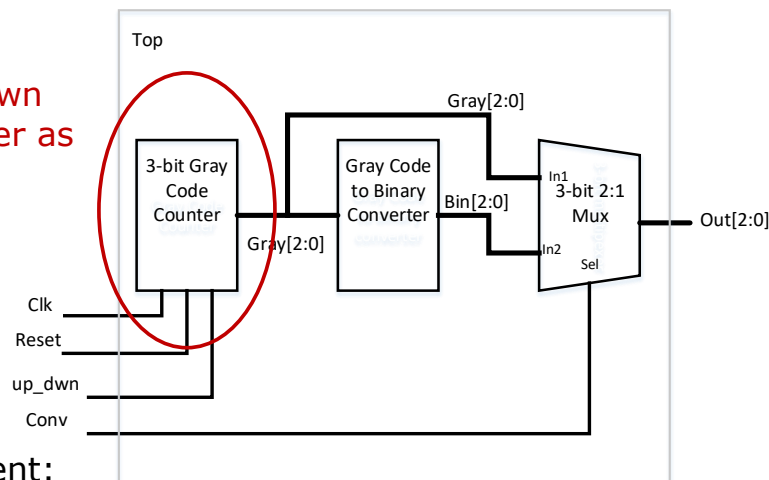Implement up/dwn
gray code counter as
an FSM



Problem statement:

Implement a gray-code counter w/ a selectable binary and gray code output

When Conv == 0 you want Out[2:0] to be the unconverted Gray Code from the counter. When Conv == 1 you want the Out[2:0] to be the Binary code from the converter. The 3-bit Up/Down Gray Code counter will be implemented as a FSM.


ECE 351 Verilog and FPGA Design

Gray Code counter state transition diagram

33

Example:

[..\examples\gray_code_cntr_mux\hdl](#)

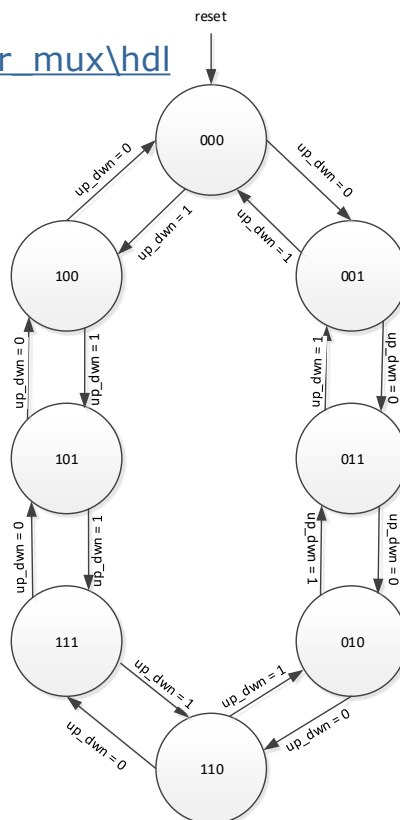

ECE 351 Verilog and FPGA Design

Next Time

- Topics:
 - Modeling sequential logic (wrap-up)
 - Avoiding unintentional latches
- You should:
 - Read Sutherland Ch 9
- Homework, projects and quizzes
 - Homework #3 will be released by Thu, 13-May. Due to D2L by 10:00 PM on Mon, 24-May