

ECE 351

Verilog and FPGA Design


Lecture 2_2: Simulating w/ QuestaSim **Exercise 1 – Putting it all together**

Roy Kravitz
Electrical and Computer Engineering Department
Maseeh College of Engineering and Computer Science



Review: Event list

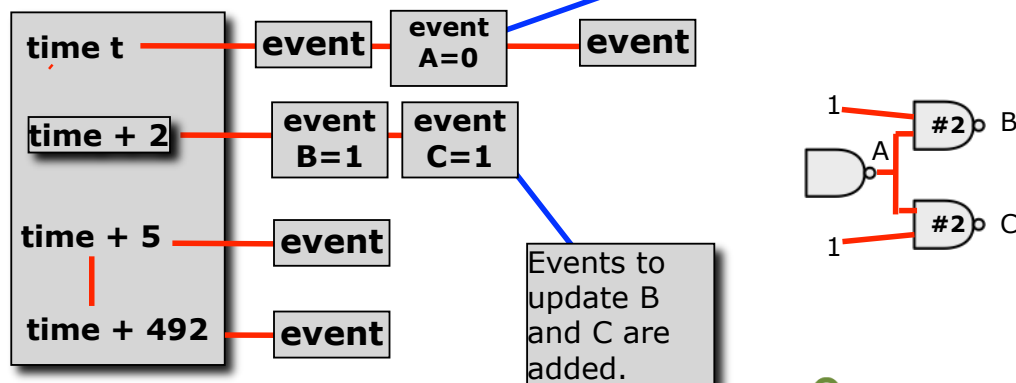- A time-ordered list of events is maintained
 - All events for a given time are kept together in an event list ordered by time
 - Events are handled at the given time and possibly schedule their output to change at a later time (a new event)
 - Here, these are update events



Pseudo Code: Event-driven simulation

put all initial and always blocks in the event list


One traversal of the while loop is a *simulation cycle*.

```

while something in time-ordered event list {
  advance simulation time to first event's time
  retrieve all events e for this time
  update state from all update-event values

  For each event e in arbitrary order {
    If it's an update event {
      follow fanout, evaluate gates there
      If an output changes
        schedule update event for it
    }
    else // it's an evaluation event
      evaluate the model
  }
}
  
```

Event scheduling

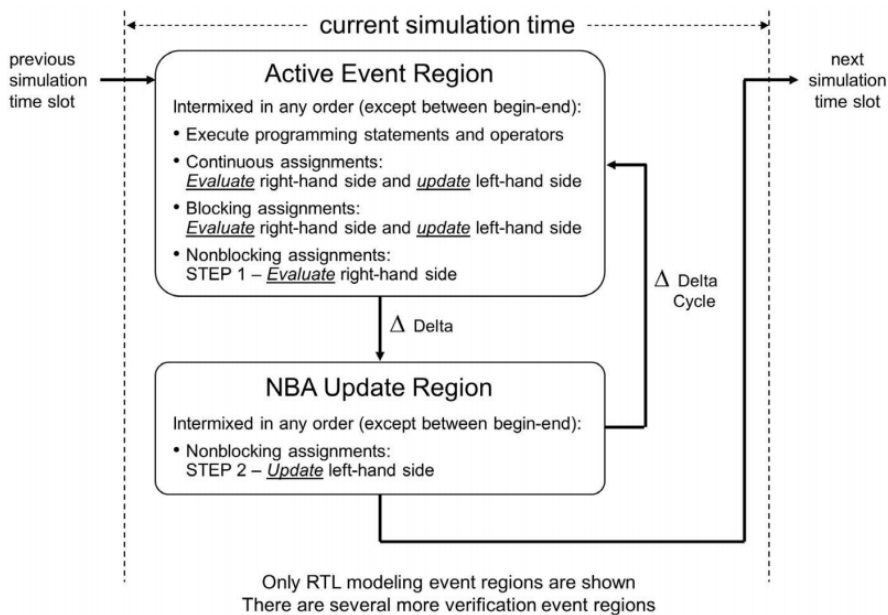

- ☐ Blocking assigns (assign $a = b$) – model combinational logic
- ☐ Non-blocking assigns ($a <= b$) – model sequential logic

Logic simulation w/ QuestaSim

Example: [..\examples\ripple_carry_counter.pdf](#)

QuestaSim Tutorial: [..\docs\Questa® SIM Tutorial.pdf](#)

Using QuestaSim at PSU: [..\docs\UsingMentorQuestaAtPSU_R2_0.pdf](#)

Some definitions

- **Module** – the basic building block in Verilog
 - Can be an element or a collection of lower-level design blocks
 - Can provide abstraction...hides the details of the implementation (i.e. possible to modify block internals without affecting the rest of the design)
- **Instance** – Module is a template, instance is the actual object
- **Simulation** – The act of applying inputs to and monitoring the outputs from a Verilog model
- There are two distinct components of a **simulation**
 - **Design Block** – the implementation of the desired functionality
 - **Stimulus Block (Test Bench or Testbench)** – The inputs applied to the **design block**

Display tasks

- Verilog supports system tasks for performing I/O, generating random numbers, initializing memory, etc.
 - Modeled after C library calls, but typically less flexible
 - All system tasks have the form `$<keyword>`
- Display tasks:
 - `$display()` – prints information on stdout w/ new line char
 - `$write()` – prints information on stdout w/o new line char
 - `$strobe()` – like `$display()` except prints at end of time step (e.g. all events have been processed)
 - `$monitor()` – continually monitors all of the arguments and prints whenever any of the signals being monitored changes

\$display()

- `$display()` - displays values of variables or strings or expressions
 - *usage*: `$display(format_desc, p1, p2, p3,...,pn);`
 - Format description is similar to C (`%d`, `%b`, etc. work)
 - Ex: `$display("ID of the port is %b", port_id);`
- You must explicitly tell Verilog to `$display` something...in other words, the `$display()` must be in a block of executable code
- Common problem: `$display()` is invoked in a situation where (simulation) time does not advance
 - Ex:

```
for (i = 0, i < 100, i = i+1)
    $display($time, x, y, z);
```
 - Simple fix: `#5 $display(...); // add some delay`

\$monitor()

- `$monitor()` - displays values of variables or strings or expressions whenever their value(s) change
 - *usage:* `$monitor(p1, p2, p3,...,pn);`
 - All the variables in the list are displayed whenever one or more of them change
 - Ex:
`$monitor($time, "clock = %b, reset = %b", clock, reset);`
 - `$monitoron`, `$monitoroff` enable and disable monitoring

Delays

- SystemVerilog simulators model the behavior of a digital system over time and support delays (specified in time units)
 - `assign #2 sum = a ^ b // #2 refers to time units`
 - Behavior: `sum` is assigned to `a ^ b` two time units after the current time whenever either `a` or `b` or both change
- You can associate time units to “physical” time using the `timeunit` and `timeprecision` statements
 - ex: `timeunit 1ns; timeprecision 100ps` (Or `timeunit 1ns/100ps`)
 - 1 time unit = 1ns, precision is 100ps (e.g., all delays rounded to 0.1ns)
 - Normally put into each module but only useful for simulation...synthesis ignores delays in the code because delays are technology-specific
 - No default defined in the spec...up to the vendor
- There are several ways to assign delays and they are dependent on context...more on this later

Delays (cont'd)

```
module decoder2x4 (
  input logic A, B, EN,
  output logic [0:3] Z
);
```

```
timeunit 1ns/1ns;
```

```
logic Abar, Bbar;
```

```
assign #1 Abar = ~A;
```

```
assign #1 Bbar = ~B
```



```
assign #2 Z[0] = ~(Abar & Bbar & EN);
```

```
assign #2 Z[1] = ~(Abar & B & EN);
```

```
assign #2 Z[2] = ~(A & Bbar & EN);
```



```
assign #2 Z[3] = ~(A & B & EN);
```

```
endmodule : decoder2x4
```

  


Testbenches

- The functionality of a design can be tested by applying **stimulus** and checking for a correct result
 - The stimulus block is commonly called a **Test Bench**
 - Test benches can be written in Verilog using the full feature set of the language
 - You can build one or more test benches, each focusing on a specific piece of functionality
 - Obvious...but worth saying – The correctness of the design depends heavily on the effectiveness of the test cases
 - Two approaches:

 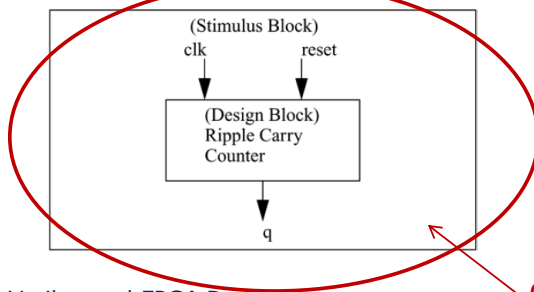

Example: 4-bit Ripple Carry Counter

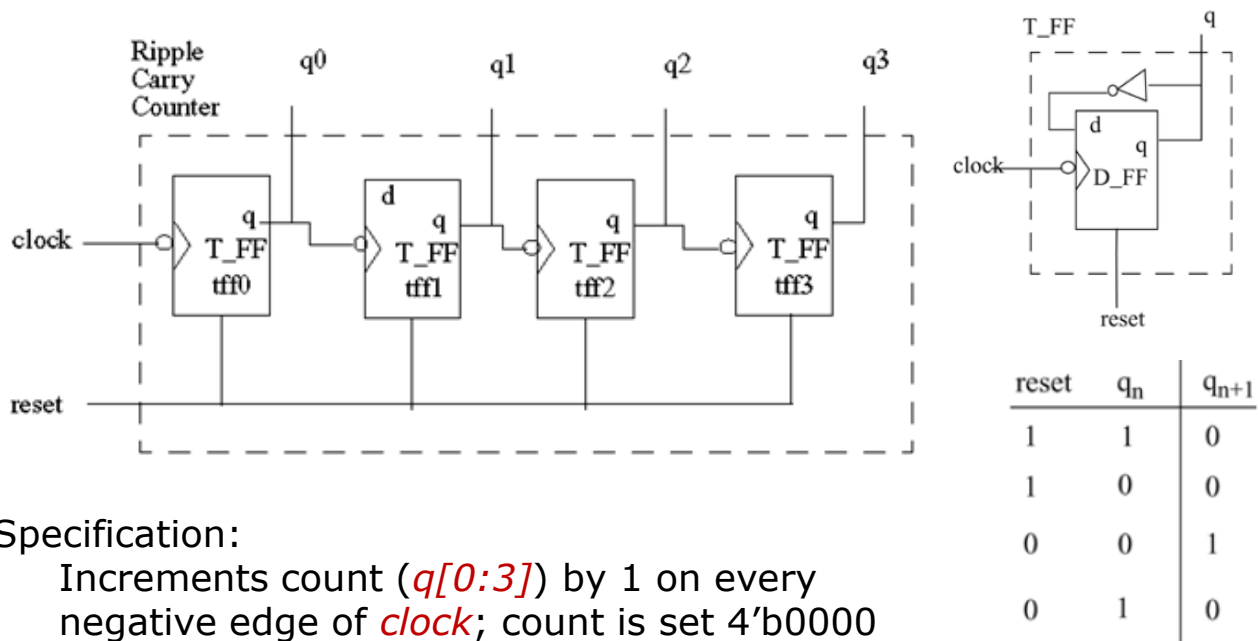


Specification:

Increments count ($q[0:3]$) by 1 on every negative edge of *clock*; count is set 4'b0000 when *reset* is asserted

Hierarchy

14

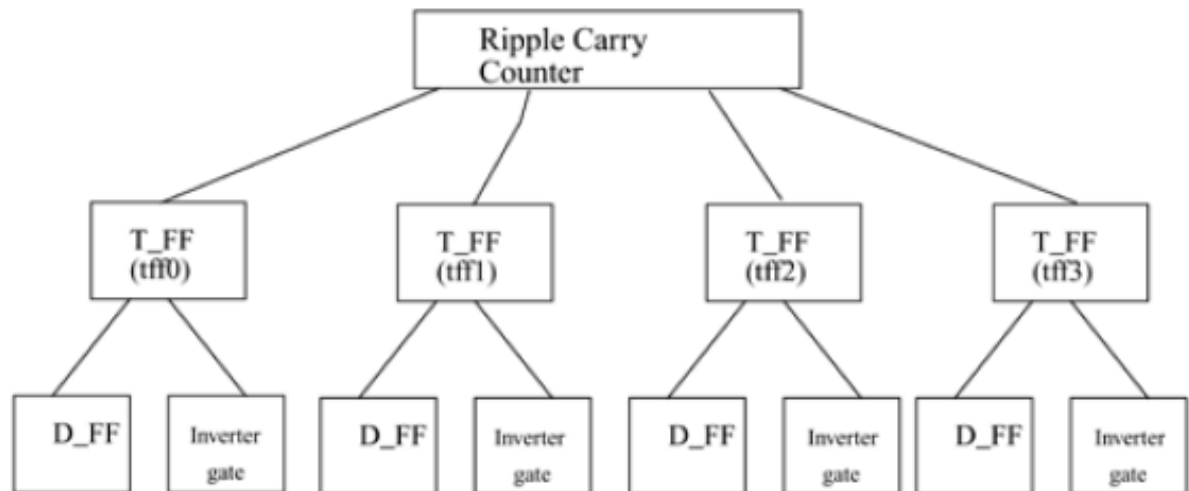


Design block – D flip-flop

```
// D flip-flop with asynchronous reset – RTL model
module DFF(
    output logic q,
    input logic d, clk, reset
);

always_ff @(negedge clk or posedge reset) begin
    if (reset)
        q <= 1'b0;
    else
        q <= d;
end

endmodule : DFF
```

 

ECE 351 Verilog and FPGA Design

Design Block – TFF Sub-block



```
// Toggle Flip-flop
module TFF (
    output logic q,
    input logic clk, reset
);

    logic d;

    // instantiate a D flip-flop
    DFF dff0(.q, .d, .clk, .reset);

    // create the toggle flip-flop by driving input with inverted output
    not n1(d, q); // not is a Verilog provided primitive.

endmodule : TFF
```

  


ECE 351 Verilog and FPGA Design

Design block – top-level


```
// Top level module for 4-bit Ripple Carry Counter
module ripple_carry_counter (
    output [3:0] count,
    input clk, reset
);
    // internal signals
    logic q0, q1, q2, q3;

    //instantiate 4 toggle flip-flops
    TFF tff0(q0,clk, reset);
    TFF tff1(q1,q0, reset);
    TFF tff2(q2,q1, reset);
    TFF tff3(q3,q2, reset);
    assign count = {q3, q2, q1, q0};

endmodule : ripple_carry_counter
```

 

ECE 351 Verilog and FPGA Design

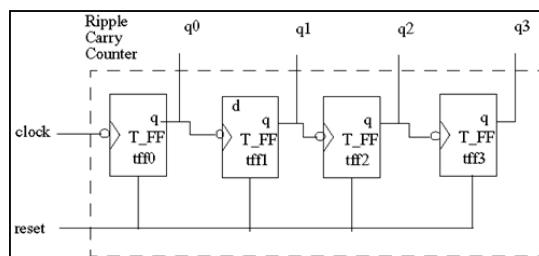

Portland State
UNIVERSITY

Source: Palnitkar, Verilog HDL, 2nd Edition

Ex: Stimulus block for Ripple Carry Counter

18

```
// Stimulus module to test the ripple carry counter
// Toggle reset and watch it count
// NOTE: There are no external ports - typical for test benches
module stimulus;
    logic clk;
    logic reset;
    logic[3:0] q;

    // instantiate the design under test (DUT)
    ripple_carry_counter DUT(.*);

    // Create the clk signal that drives the design block.
    initial begin
        clk = 1'b0;
    end // initial block

    always begin
        #5 clk = ~clk;
    end // always block

    ...
endmodule
```


Ex: Stimulus Block for Ripple Carry Counter ¹⁹

```
// Monitor the outputs
initial begin
    $monitor($time, " Output q = %d",  q);
end

// Control the reset signal that drives the design block
initial begin : test_vectors
    #0  reset = 1'b1;
    #15  reset = 1'b0;
    #180 reset = 1'b1;
    #10  reset = 1'b0;
    #20  $stop;
end : test_vectors
endmodule : stimulus
```


Using the QuestaSim GUI

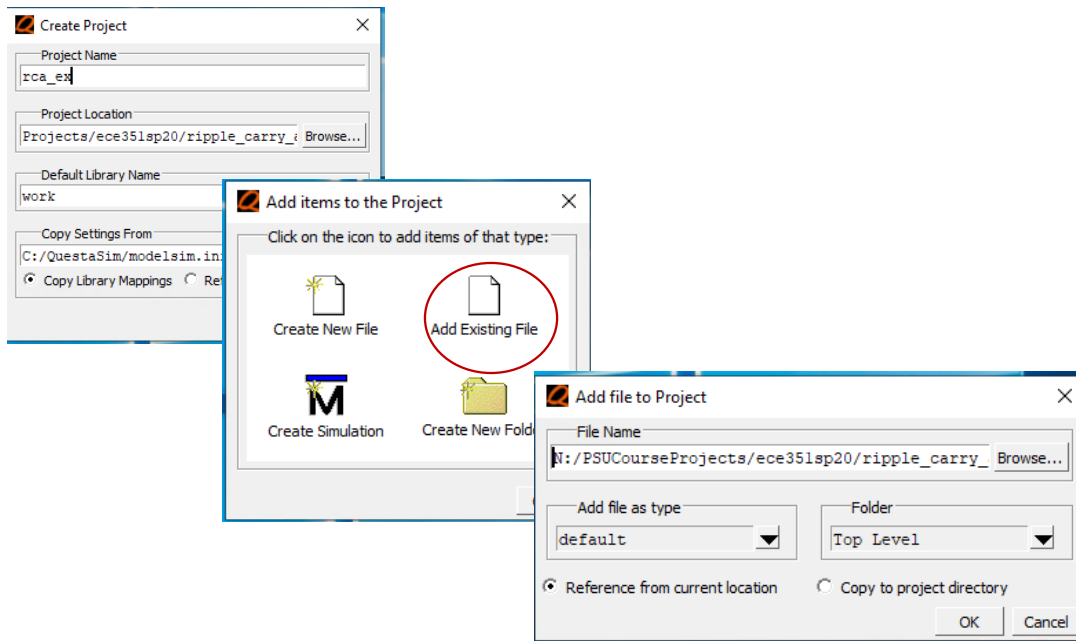Create a new QuestaSim Project and add the source files
File/New Project...



Using the QuestaSim GUI (cont'd)

 
Compile the source files
Compile/Compile All



Using the QuestaSim GUI (cont'd)


Load the simulation model

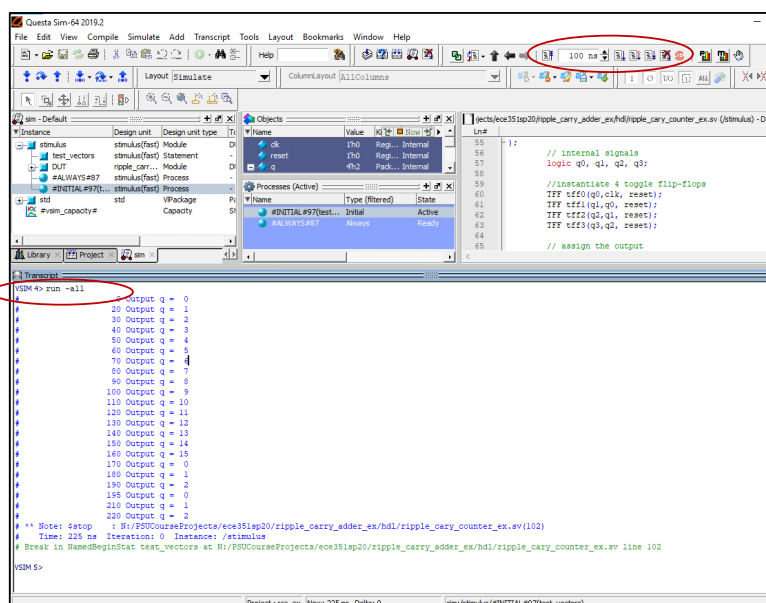Select Library tab, open work directory, select top module, right click and select Simulate




Using the QuestaSim GUI (cont'd)

Run the simulation

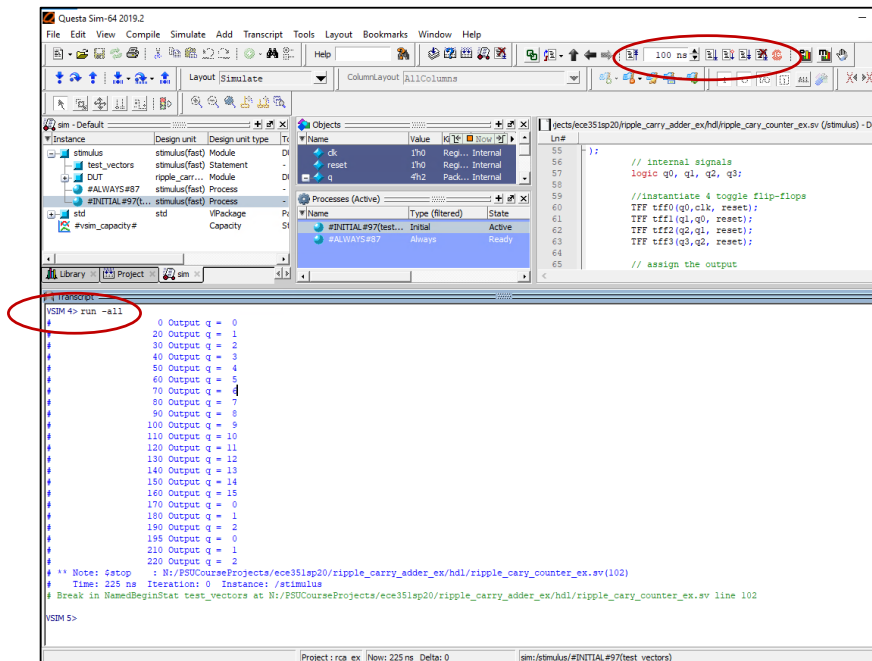

Using the QuestaSim GUI (cont'd)

 


Exercise 1 - Putting it all together (implementing an 8-bit ripple-carry adder)

Steps:

- Create a gate-level module for a single-bit full adder
- Create a 4-bit ripple carry adder by instantiating and connecting 4 single-bit full adders
- *Create an 8-bit ripple carry adder DUT by instantiating and connecting two instances of the 4-bit ripple carry adder*
- *Simulate your design with the testbench I provided*
- *Submit your source code and a transcript showing your simulation results to your Exercise 1 dropbox on D2L*
 - *Due to D2L by 5:00 PM on Friday*

Single-bit full adder schematic

 

Write a SystemVerilog module (file: `fa.sv`) that implements this schematic using gate-level modeling


Single-bit full adder module starter code

```
//////////////////////////////////////////
// fa.sv - Single bit full adder
//
// author:  <name> (<email address>)
//////////////////////////////////////////
module FA (
    input logic A, B, Cin,      // a, b, and carry_in inputs
    output logic S, Cout        // sum and carry out outputs
);

// ADD YOUR CODE HERE

endmodule : FA
```

4-bit Ripple Carry Adder

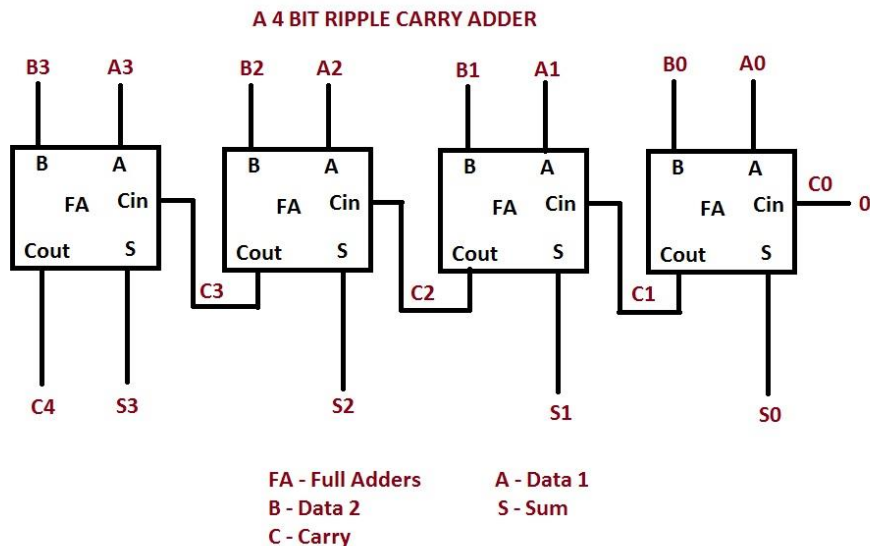

Write a SystemVerilog module (file: `adder_4bits.sv`) that implements this schematic by instantiating 4 instances of FA and connecting the inputs and outputs.

4-bit adder module starter code


```
//////////////////////////////////////////
// adder_4bits.sv - 4 bit adder
//
// Author:  <name> (<email address>)
//////////////////////////////////////////
module adder_4bits (
    input logic [3:0] A, B,
    input logic C0,
    output logic [3:0] S,
    output logic C4
);

// internal variables
wire C1, C2, C3;

// instantiate and connect four FA's
// ADD YOUR CODE HERE

endmodule: adder_4bits
```

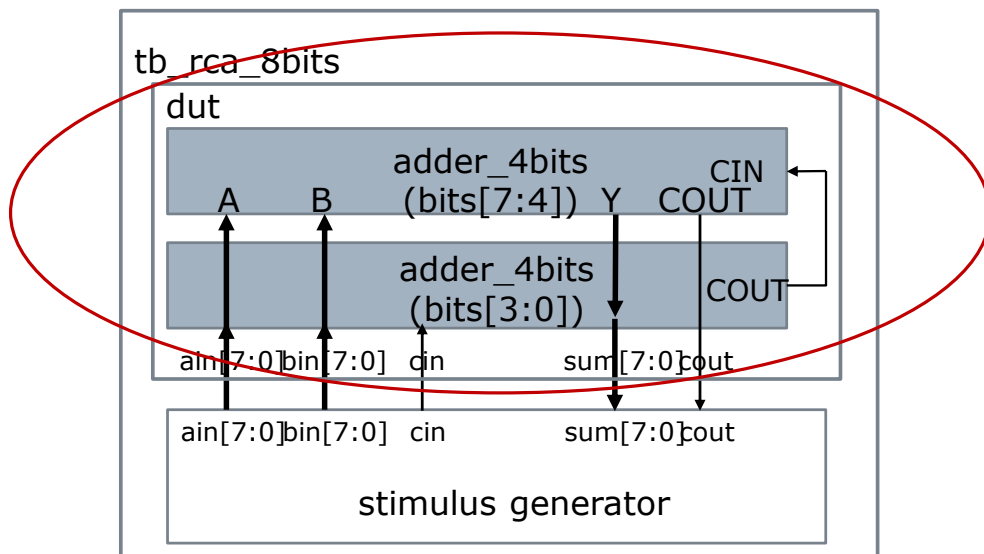Top level 8-bit ripple carry adder (the DUT) ³⁰



Write a SystemVerilog module (file: `dut.sv`) that instantiates and connects to `adder_4bits`

Top level starter code


```
////////////////////////////////////////
// dut.sv - 8-bit Ripple Carry Adder
//
// Author:  <name> (<email address>)
////////////////////////////////////////
module dut (
    input logic [7:0] ain, bin,
    input logic cin,
    output logic [7:0] sum,
    output logic cout
);

timeunit 1ns/1ns;

// ADD YOUR CODE HERE

endmodule: dut
```

Simulate your design

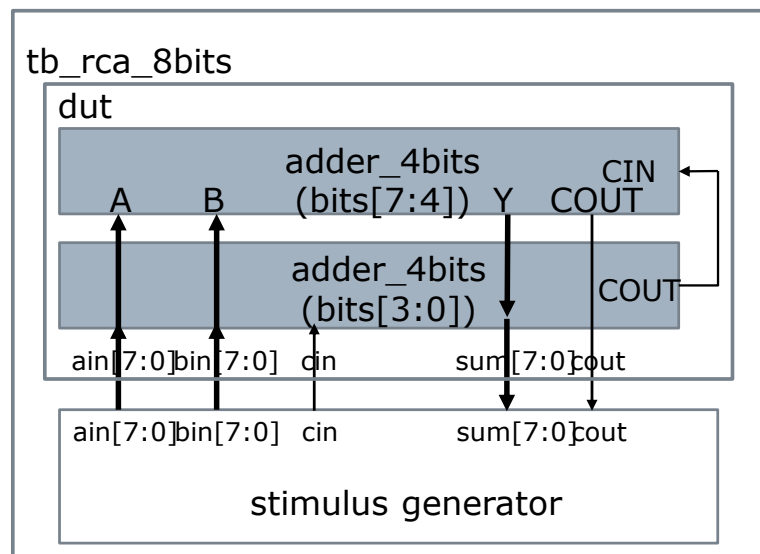

Build a project in QuestaSim and simulate your design. Submit your SystemVerilog source code and a transcript of your successful simulation to D2L by Noon on Friday

Next Time

- ☐ Topics:
 - Exercise 1 solution
 - Packed and unpacked arrays
 - Parameters and constants
- ☐ You should:
 - Finish writing, simulate and submit your “in-class” exercise results to D2L (worth up to 20 pts)
 - ☐ Include the SystemVerilog code that you wrote and a transcript showing your simulation results.
 - ☐ Put all of the files and the transcript in a single .zip or rar file named <yourname>_exercise1 (ex: rkravitz_exercise1.zip)
 - ☐ Deadline is 5:00 PM on Friday 09-April
- ☐ Homework, projects and quizzes
 - Homework #1 will be assigned Tue, 13-Apr