

ECE 351

Verilog and FPGA Design

Week 7_2: Modeling sequential logic (wrap-up)
Avoiding unintended latches


Roy Kravitz
Electrical and Computer Engineering Department
Maseeh College of Engineering and Computer Science

Finite State Machines

Sources:



- Roy's lecture notes from days long past (2003 – 2004)
- *Fundamentals of Digital Logic with Verilog 1st Edition*, Stephen Brown and Zvonko Vranesic, McGraw-Hill, 2003

Sequential circuits - general form

 

- A Sequential circuit is a circuit where the outputs depend on past behavior and the present value of the inputs
- A Synchronous sequential circuit is a sequential circuit where a clock signal is used to control the sequencing
- A Sequential circuit of this form is also called a Finite State Machine (FSM)

Mealy and Moore machines

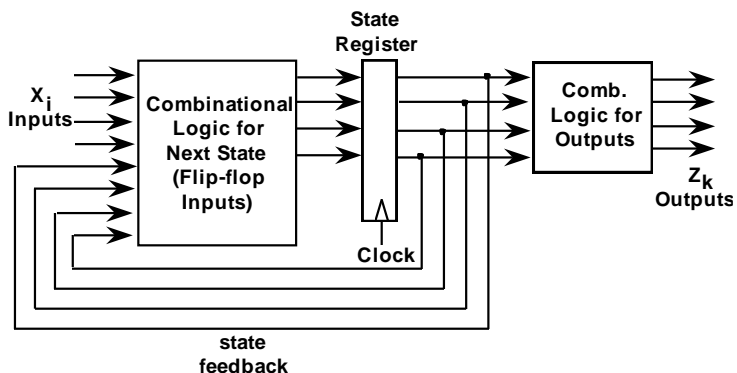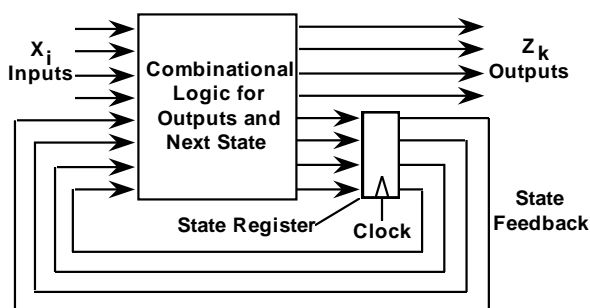

Mealy Machine

- ☐ Outputs depend on state AND inputs
- ☐ Input change causes an immediate output change
- ☐ Asynchronous signals

Moore Machine

- ☐ Outputs are function solely of the current state
- ☐ Outputs change synchronously with state changes

Our first FSM design (FSM)

Step 1: Understand the specification

□ Specification:


- The circuit has one input w and one output z
- All changes occur on the positive edge of a clock signal
- The output z is equal to 1 if during two immediately preceding clock cycles the input w was equal to 1. Otherwise, $z = 0$;

Sample Sequence:

Clockcycle:	t0	t1	t2	t3	t4	t5	t6	t7	t8	t9	t10
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0


Our first FSM design example (cont'd)

Step 2: Draw a State transition diagram

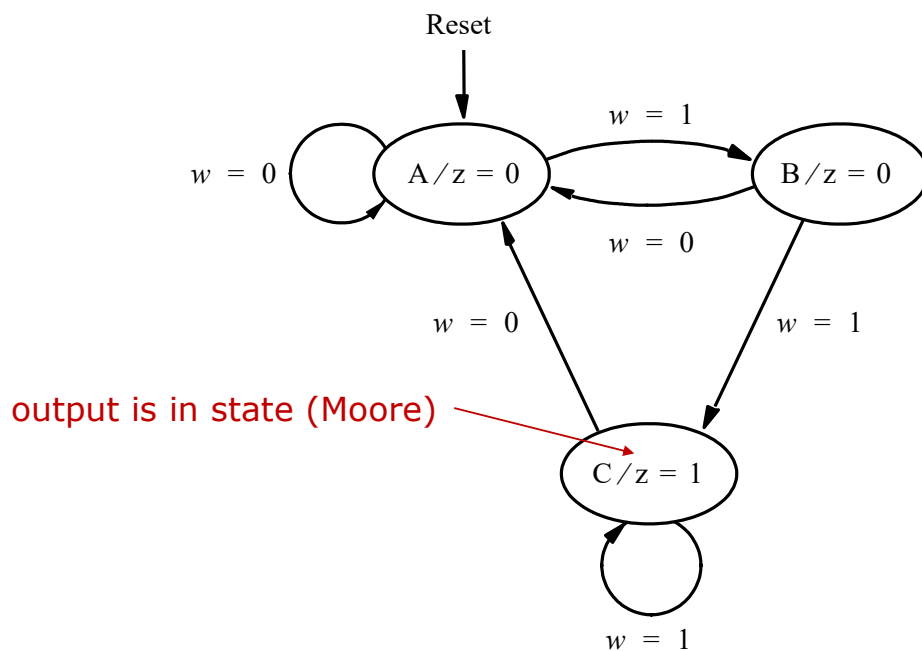

Our first FSM design example (cont'd)

 Step 3: Map the State transition diagram to a state table



Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

Our first FSM design example (cont'd)

Step 4b: Create the State Assigned table


Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

A
B
C

Present state $y_2 y_1$	Next state		Output z
	$w = 0$	$w = 1$	
	$Y_2 Y_1$	$Y_2 Y_1$	
00	00	01	0
01	00	10	0
10	00	10	1
11	<i>dd</i>	<i>dd</i>	<i>d</i>

Our First FSM Design Example (cont'd)

Step 4c: Map the State Table to hardware

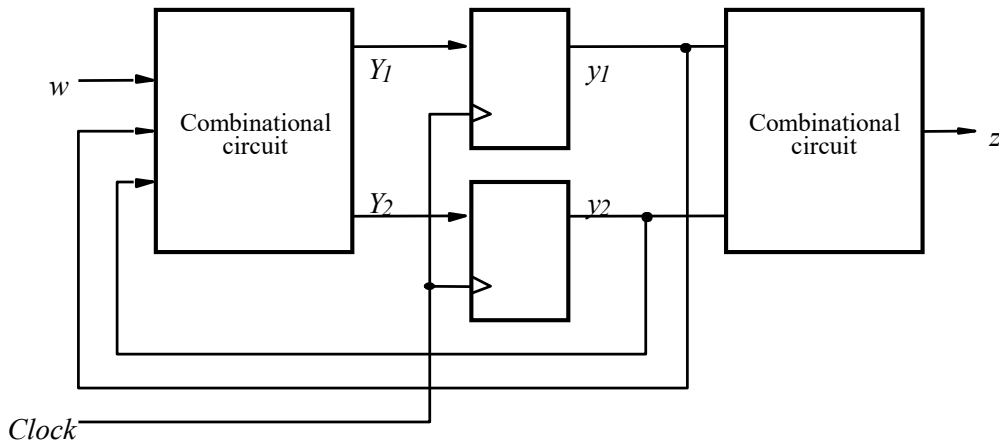

Step 4d: Use K-maps, alternate state mappings, etc. to minimize logic

Step 5: Draw schematics

Write the SystemVerilog

```

module firstFSMEx (
    input logic clock, resetn, w,
    output logic z
);
    logic [2:1] y, Y;
    enum logic [1:0]{A = 2'b00,
                    B = 2'b01,
                    C = 2'b10};

    // next state logic (comb. block)
    always_comb
        case (y)
            A: if (w) Y = B;
               else Y = A;

            B: if (w) Y = C;
               else Y = A;

            C: if (w) Y = C;
               else Y = A;

            default: Y = 2'bxx;
        endcase

    // Define the sequential block
    always_ff @(posedge clock or negedge resetn)
        if (resetn == 0)
            y <= A;
        else
            y <= Y;

    // Define output
    assign z = (y == C);
endmodule: firstFSMEx

```

Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	C	1

Another way

```

module firstFSMEx (
    input logic clock, resetn, w,
    output logic z
);
    logic [2:1] y, Y;
    enum logic [1:0] {A = 2'b00,
                     B = 2'b01,
                     C = 2'b10};

    // next state logic (comb. block)
    always_comb
    case (y)
        A: if (w) Y = B;
           else Y = A;

        B: if (w) Y = C;
           else Y = A;

        C: if (w) Y = C;
           else Y = A;

        default: Y = 2'bxx;
    endcase

    // output logic (comb. block)
    always_comb
    case (y)
        A: z = 1'b0;
        B: z = 1'b0;
        C: z = 1'b1;
        default: z = 1'bx;
    endcase

    // Define the sequential block
    always_ff @(posedge clock or negedge resetn)
        if (resetn == 0)
            y <= A;
        else
            y <= Y;
    endmodule: firstFSMEx

```

Yet another way

```

module firstFSMEx (
    input logic clock, resetn, w
    output logic z
);
    logic [2:1] y, Y;
    enum logic [1:0] {A = 2'b00,
                     B = 2'b01,
                     C = 2'b10};

    // Define the sequential block
    always_ff @(posedge clock or negedge resetn)
        if (resetn == 0)
            y <= A
        else
            case (y)
                A: if (w) y <= B else y <= A;
                B: if (w) y <= C else y <= A;
                C: if (w) y <= C else y <= A;
                default: y <= 2'bxx;
            endcase


    // Define output
    assign z = (y == C);
endmodule: firstFSMEx

```

Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	C	1

Mealy state model

Clockcycle:	t0	t1	t2	t3	t4	t5	t6	t7	t8	t9	t10
w:	0	1	0	1	1	0	1	1	1	0	1
z:	0	0	0	0	0	1	0	0	1	1	0

 


output is in transition (Mealy)

Mealy state model (cont'd)


Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

Present state	Next state		Output	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
y	Y	Y	z	z
A	0	1	0	0
B	1	1	0	1

Mealy implementation

 

(a) Circuit

 

(b) Timing diagram

Write the SystemVerilog

```
module firstFSMEx (  
    input logic clock, resetn, w,  
    output logic z  
);  
    logic y;  
  
    // Define the sequential block  
    always_ff @(posedge clock or negedge resetn)  
        if (resetn == 0)  
            y <= 1'b0  
        else  
            y <= w;  
  
    // Define output block  
    always_comb  
        z = w & y;  
  
endmodule
```


Coding to avoid unintentional latches

Sources:

- RTL Modeling with System Verilog for Simulation and Synthesis, Stuart Sutherland

Inferring latches

Synthesis will infer a latch whenever a non-clocked always block is entered and there is a possibility that one or more of the variables used on the LHS of an assignment will not be updated

Two reasons:

- Incomplete decision statements
 - Does not have a decision branch for every possible value of the decision expression
 - Can occur with either `if..else` and `case` statements
- Incomplete decision branches
 - Does not make assignments to all of the variables that are outputs of the procedure

Can occur anywhere in the RTL models where `if..else` or `case` statements are used

Examples of inferring latches (cont'd)

Incomplete decision statements

```
always_comb begin // 3-to-1 multiplexor
  case (select)
    2'b00: y = a;
    2'b01: y = b;
    2'b10: y = c;
  endcase
end
```

Incomplete decision branches

```
always_comb begin // add or subtract
  case (mode)
    1'b0: add_result = a + b;
    1'b1: subtract_result = a - b;
  endcase
end
```

Inadvertent latches in state machine models

```
always_comb begin
  case (current_state) // 5 states, binary count encoding
    3'b000: control_bus = 4'b0000;
    3'b001: control_bus = 4'b1010;
    3'b011: control_bus = 4'b1110;
    3'b100: control_bus = 4'b0110;
    3'b101: control_bus = 4'b0101;
  endcase
end
```

```
always_comb begin
  case (1'b1) // 5 states, one-hot encoding
    current_state[0]: control_bus = 4'b0110;
    current_state[1]: control_bus = 4'b1010;
    current_state[2]: control_bus = 4'b1110;
    current_state[3]: control_bus = 4'b0110;
    current_state[4]: control_bus = 4'b0101;
  endcase
end
```


Avoiding inferred latches

- Best practice is to avoid them by fully specifying all of the output values of decision statements for all the possible decision branches

But if you can't...or decide not to:

- Five common coding styles:
 - Use a default case item to assign known output values
 - Use a pre-case assignment before the case statement that assigns known known output values
 - Use the unique and priority decision modifiers
 - ~~Use the obsolete...and dangerous...full_case_synthesis~~
 - ~~Use an X assignment value to indicate don't care conditions~~

Example 9.2

 

```

module simple_fsm
(input logic clk, rstN,
output logic get_ready, get_set, get_going
);

typedef enum logic [2:0] {RESET = 3'b000, // Johnson Count
READY = 3'b001,
SET = 3'b011,
GO = 3'b111} states_t;

states_t current_state, next_state;

// state sequencer
always_ff @(posedge clk or negedge rstN) // async reset
if (!rstN) current_state <= RESET; // active-low reset
else current_state <= next_state;

// next state decoder
always_comb begin
case (current_state)
RESET : next_state = READY;
READY : next_state = SET;
SET : next_state = GO;
GO : next_state = READY;
endcase
end

// output decoder
always_comb begin
case (current_state)
READY : get_ready = '1;
SET : get_set = '1;
GO : get_going = '1;
endcase
end
endmodule: simple_fsm

```

Style 1: Default case item w/ known values

```
// next state decoder
always_comb begin
  case (current_state)
    RESET : next_state = READY;
    READY : next_state = SET;
    SET    : next_state = GO;
    GO     : next_state = READY;
  endcase
end
```

```
always_comb begin
  case (current_state)
    RESET : next_state = READY;
    READY : next_state = SET;
    SET    : next_state = GO;
    GO     : next_state = READY;
    default: next_state = RESET; // reset if error
  endcase
end
```

Style 2: Pre-case assignment, known values ²³

```
// next state decoder
always_comb begin
  case (current_state)
    RESET : next_state = READY;
    READY : next_state = SET;
    SET    : next_state = GO;
    GO     : next_state = READY;
  endcase
end
```

```
// output decoder (using pre-case assignment)
always_comb begin
  {get_ready, get_set, get_going} = 3'b000; // clear bits
  case (current_state)
    READY : get_ready = '1;
    SET    : get_set   = '1;
    GO     : get_going = '1;
  endcase
end
```

```
always_comb begin
  next_state = RESET; // default to reset if invalid state
  case (current_state)
    RESET : next_state = READY;
    READY : next_state = SET;
    SET    : next_state = GO;
    GO     : next_state = READY;
  endcase
end
```


Style 3: unique and priority modifiers

```
// next state decoder
always_comb begin
  case (current_state)
    RESET : next_state = READY;
    READY : next_state = SET;
    SET    : next_state = GO;
    GO     : next_state = READY;
  endcase
end
```

```
always_comb begin
  unique case (current_state)
    RESET : next_state = READY;
    READY : next_state = SET;
    SET    : next_state = GO;
    GO     : next_state = READY;
  endcase
end
```

Let's write some code for a FSM

A more complex pattern recognizer

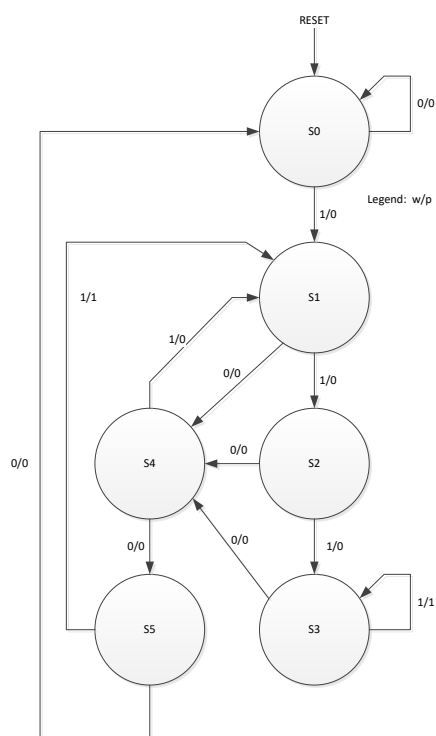

A pattern recognizer state machine has a single input w and an output p . The pattern recognizer should generate $p = 1$ when the previous 4 values of w were 1001 or 1111; otherwise, $p = 0$. Overlapping input patterns are allowed and should generate the correct output.

An example of the desired behavior for the state machine is:

w : 010111100110011111

p : 000000100100010011

The inputs to the module are w , $clock$, and $reset$. There is one output, p .

Next Time

- Topics:
 - Functions and tasks
 - Review midterm exam solutions
- You should:
 - Review Sutherland Ch 6 (Functions and Tasks)
 - Read Sutherland Ch 9
- Homework, projects and quizzes
 - Homework #3 will be released Thu, 13-May. Due to D2L by 10:00 PM on Mon, 24-May